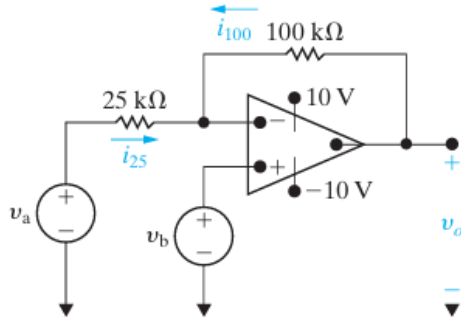


**EXAMPLE 5.1****Analyzing an Op Amp Circuit**

The op amp in the circuit shown in Fig. 5.7 is ideal.

- Calculate  $v_o$  if  $v_a = 1$  V and  $v_b = 0$  V.
- Repeat (a) for  $v_a = 1$  V and  $v_b = 2$  V.
- If  $v_a = 1.5$  V, specify the range of  $v_b$  that avoids amplifier saturation.



**Figure 5.7** ▲ The circuit for Example 5.1.

**Solution**

- a) **Step 1:** A negative feedback path exists from the op amp's output to its inverting input through the  $100\text{ k}\Omega$  resistor, so we assume the op amp is confined to its linear operating region.

**Step 2:** The voltage at the inverting input terminal is 0 because  $v_p = v_b = 0$  from the connected voltage source, and  $v_n = v_p$  from the voltage constraint in Eq. 5.2.

**Step 3:** Use KCL to sum the currents entering the node labeled  $v_n$  to get

$$i_{25} + i_{100} - i_n = 0.$$

Remember that  $i_n$  is the current entering the inverting op amp terminal. From Ohm's law,

$$i_{25} = \frac{v_a - v_n}{25,000} = \frac{1 - 0}{25,000} = \frac{1}{25,000};$$

$$i_{100} = \frac{v_o - v_n}{100,000} = \frac{v_o - 0}{100,000} = \frac{v_o}{100,000}.$$

The current constraint requires  $i_n = 0$ . Substituting the values for the three currents into the KCL equation, we obtain

$$\frac{1}{25} + \frac{v_o}{100} = 0.$$

Hence,  $v_o$  is  $-4$  V.

**Step 4:** Because  $v_o$  lies between  $\pm 10$  V, our assumption that the op amp is in its linear region of operation is confirmed.

- b) Using the same steps as in (a), we get

$$v_p = v_b = v_n = 2\text{ V},$$

$$i_{25} = -i_{100}.$$

$$i_{25} = \frac{v_a - v_n}{25,000} = \frac{1 - 2}{25,000} = -\frac{1}{25,000};$$

$$i_{100} = \frac{v_o - v_n}{100,000} = \frac{v_o - 2}{100,000}.$$

Therefore,  $v_o = 6$  V. Again,  $v_o$  lies within  $\pm 10$  V.

- c) As before,  $v_n = v_p = v_b$ , and  $i_{25} = -i_{100}$ . Because  $v_a = 1.5$  V,

$$\frac{1.5 - v_b}{25,000} = \frac{v_o - v_b}{100,000}.$$

Solving for  $v_b$  as a function of  $v_o$  gives

$$v_b = \frac{1}{5}(6 + v_o).$$

Now, if the amplifier operates within its linear region,  $-10\text{ V} \leq v_o \leq 10\text{ V}$ . Substituting these limits on  $v_o$  into the expression for  $v_b$ , we find the range for  $v_b$  is

$$-0.8\text{ V} \leq v_b \leq 3.2\text{ V}.$$

### EXAMPLE 5.2 Designing an Inverting Amplifier

- a) Design an inverting amplifier (see Fig. 5.8) with a gain of 12. Use  $\pm 15$  V power supplies and an ideal op amp.
- b) What range of input voltages,  $v_s$ , allows the op amp in this design to remain in its linear operating region?

#### Solution

- a) We need to find two resistors whose ratio is 12 from the realistic resistor values listed

in Appendix H. There are lots of different possibilities, but let's choose  $R_s = 1 \text{ k}\Omega$  and  $R_f = 12 \text{ k}\Omega$ . Use the inverting-amplifier equation (Eq. 5.4) to verify the design:

$$v_o = -\frac{R_f}{R_s} v_s = -\frac{12,000}{1,000} v_s = -12v_s.$$

Thus, we have an inverting amplifier with a gain of 12, as shown in Fig. 5.10.

The Operational Amplifier

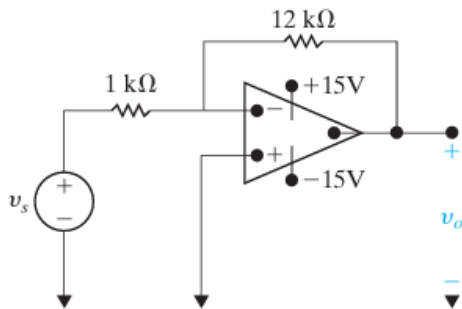


Figure 5.10 ▲ Inverting amplifier for Example 5.2.

- b) Solve two different versions of the inverting-amplifier equation for  $v_s$ , first using  $v_o = +15$  V and then using  $v_o = -15$  V:

$$15 = -12v_s \text{ so } v_s = -1.25 \text{ V};$$

$$-15 = -12v_s \text{ so } v_s = 1.25 \text{ V}.$$

Thus, if the input voltage is greater than or equal to  $-1.25$  V and less than or equal to  $+1.25$  V, the op amp in the inverting amplifier will remain in its linear operating region.

### EXAMPLE 5.3 Designing a Summing Amplifier

- a) Design a summing amplifier (see Fig. 5.11) whose output voltage is

$$v_o = -4v_a - v_b - 5v_c.$$

Use an ideal op amp with  $\pm 12$  V power supplies and a  $20\text{ k}\Omega$  feedback resistor.

- b) Suppose  $v_a = 2$  V and  $v_c = -1$  V. What range of input voltages for  $v_b$  allows the op amp in this design to remain in its linear operating region?
- c) Suppose  $v_a = 2$  V,  $v_b = 3$  V, and  $v_c = -1$  V. Using the input resistor values found in part (a), how large can the feedback resistor be before the op amp saturates?

#### Solution

- a) Use the summing-amplifier equation (Eq. 5.6) and the feedback resistor value to find the three input resistor values:

$$-\frac{R_f}{R_a} = -4 \quad \text{so} \quad R_a = \frac{20\text{ k}}{4} = 5\text{ k}\Omega;$$

$$-\frac{R_f}{R_b} = -1 \quad \text{so} \quad R_b = \frac{20\text{ k}}{1} = 20\text{ k}\Omega;$$

$$-\frac{R_f}{R_c} = -5 \quad \text{so} \quad R_c = \frac{20\text{ k}}{5} = 4\text{ k}\Omega.$$

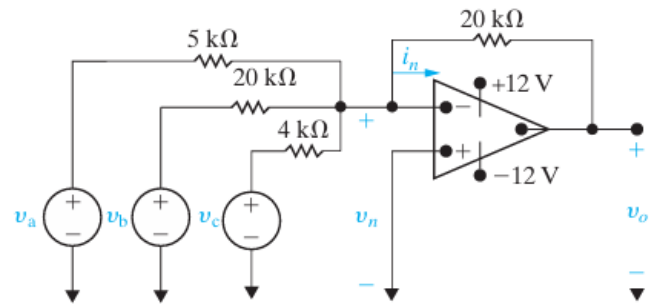


Figure 5.12 ▲ The summing amplifier for Example 3.3(a).

The resulting circuit is shown in Fig. 5.12.

- b) Substitute the values for  $v_a$  and  $v_c$  into the equation for  $v_o$  given in the problem statement to get

$$v_o = -4(2) - v_b - 5(-1) = -3 - v_b.$$

Solving this equation for  $v_b$  in terms of  $v_o$  gives

$$v_b = -3 - v_o.$$

Now substitute the two power supply voltages for the output voltage to find the range of  $v_b$  values that keeps the op amp in its linear region:

$$-15\text{ V} \leq v_b \leq 9\text{ V}.$$

- c) Starting with the summing-amplifier equation, Eq. 5.6, substitute the input resistor values found in part (a) and the specified input voltage values.

#### The Operational Amplifier

Remember that the feedback resistor is an unknown in this equation:

$$v_o = -\frac{R_f}{5000}(2) - \frac{R_f}{20,000}(3) - \frac{R_f}{4000}(-1) = -\frac{6R_f}{20,000}.$$

From this equation, it should be clear that if the op amp saturates, it will do so at its negative power supply value,  $-12$  V. Using this voltage

for  $v_o$  in the above equation and solving for the feedback resistance gives

$$R_f = 40\text{ k}\Omega.$$

Given the specified input voltages, this is the largest value of feedback resistance that keeps the op amp in its linear region.

**EXAMPLE 5.4****Designing a Noninverting Amplifier**

- a) Design a noninverting amplifier (see Fig. 5.13) with a gain of 6. Assume the op amp is ideal.
- b) Suppose we wish to amplify a voltage  $v_g$ , where  $-1.5 \text{ V} \leq v_g \leq +1.5 \text{ V}$ . What are the smallest power supply voltages that could be used with the resistors selected in part (a) to ensure that the op amp remains in its linear region?

**Solution**


- a) Using the noninverting-amplifier equation (Eq. 5.7),

$$v_o = \frac{R_s + R_f}{R_s} v_g = 6v_g \quad \text{so} \quad \frac{R_s + R_f}{R_s} = 6.$$

Therefore,

$$R_s + R_f = 6R_s, \quad \text{so} \quad R_f = 5R_s.$$

Look at the realistic resistor values listed in Appendix H. Let's choose  $R_f = 10 \text{ k}\Omega$ , so  $R_s = 2 \text{ k}\Omega$ . But there is not a  $2 \text{ k}\Omega$  resistor in Appendix H. We can create an equivalent  $2 \text{ k}\Omega$  resistor by combining two  $1 \text{ k}\Omega$  resistors in series. We can use a third  $1 \text{ k}\Omega$  resistor for  $R_g$ . The resulting circuit is shown in Fig. 5.14.

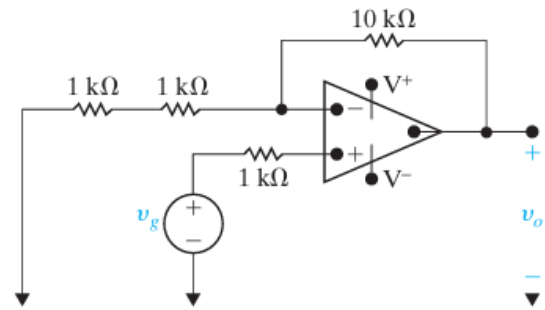

**Figure 5.14** ▲ The noninverting amplifier design of Example 5.3.

- b) Solve two different versions of the noninverting-amplifier equation for  $v_o$ , first using  $v_g = +1.5 \text{ V}$  and then using  $v_g = -1.5 \text{ V}$ :

$$v_o = 6(1.5) = 9 \text{ V};$$

$$v_o = 6(-1.5) = -9 \text{ V}.$$

Thus, if we use  $\pm 9 \text{ V}$  power supplies for the noninverting amplifier designed in part (a) and  $-1.5 \text{ V} \leq v_g \leq +1.5 \text{ V}$ , the op amp will remain in its linear operating region. The circuit resulting from the analysis in parts (a) and (b) is shown in Fig. 5.14, with  $V^+ = 9 \text{ V}$  and  $V^- = -9 \text{ V}$ .

**EXAMPLE 5.5****Designing a Difference Amplifier**

- a) Design a difference amplifier (see Fig. 5.15) that amplifies the difference between two input voltages by a gain of 8, using an ideal op amp and  $\pm 8$  V power supplies.
- b) Suppose  $v_a = 1$  V in the difference amplifier designed in part (a). What range of input voltages for  $v_b$  will allow the op amp to remain in its linear operating region?

**Solution**


- a) Using the simplified difference-amplifier equation (Eq. 5.10),

$$v_o = \frac{R_b}{R_a} (v_b - v_a) = 8(v_b - v_a) \text{ so } \frac{R_b}{R_a} = 8.$$

We want two resistors whose ratio is 8. Look at the realistic resistor values listed in Appendix H. Let's choose  $R_b = 12 \text{ k}\Omega$ , so  $R_a = 1.5 \text{ k}\Omega$ , although there are many other possibilities. Note that the simplified difference-amplifier equation requires that

$$\frac{R_a}{R_b} = \frac{R_c}{R_d}.$$

A simple choice for  $R_c$  and  $R_d$  is  $R_c = R_a = 1.5 \text{ k}\Omega$  and  $R_d = R_b = 12 \text{ k}\Omega$ . The resulting circuit is shown in Fig. 5.16.

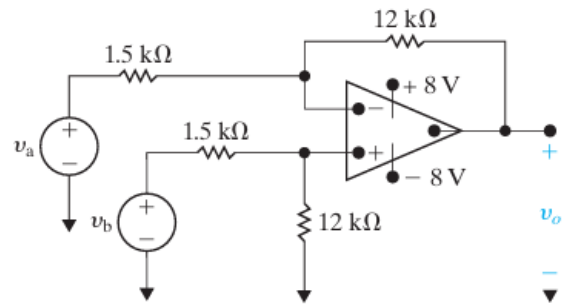

**Figure 5.16** ▲ The difference amplifier designed in Example 5.4.

- b) Using  $v_a = 1$ , solve two different versions of the simplified difference-amplifier equation (Eq. 5.10) for  $v_b$  in terms of  $v_o$ . Then substitute the two limiting values for the output voltage,  $v_o = +8$  V and  $v_o = -8$  V:

$$v_b = \frac{v_o}{8} + 1 = \frac{8}{8} + 1 = 2 \text{ V};$$

$$v_b = \frac{v_o}{8} + 1 = \frac{-8}{8} + 1 = 0 \text{ V}.$$

Thus, if  $v_a = 1$  V in the difference amplifier from part (a), the op amp will remain in its linear region if  $0 \text{ V} \leq v_b \leq 2 \text{ V}$ .

**EXAMPLE 5.6****Calculating the CMRR**

- a) Suppose the  $R_c$  resistor in the difference amplifier designed in Example 5.5, shown in Fig. 5.16, is 10% larger than its nominal value. All other resistor values are unchanged. Calculate the common mode gain, the difference mode gain, and the CMRR for the difference amplifier.
- b) Repeat part (a) assuming the  $R_d$  resistor value is 10% larger than its nominal value and all other resistor values are unchanged.

**Solution**

- a) Use the common mode gain equation in Eq. 5.15 with  $R_c = 1500(1.1) = 1650 \Omega$  to get

$$A_{cm} = \frac{(1500)(12,000) - (12,000)(1650)}{1500(1650 + 12,000)} \\ = -0.0879.$$

Then use the difference mode gain equation in Eq. 5.15 with  $R_c = 1500(1.1) = 1650 \Omega$  to get

$$A_{dm} = \frac{12,000(1500 + 12,000) + 12,000(1650 + 12,000)}{2(1500)(1650 + 12,000)} \\ = 7.956.$$

The CMRR (Eq. 5.20) is thus

$$\text{CMRR} = \left| \frac{7.956}{-0.0879} \right| = 90.5.$$

- b) Use the common mode gain equation in Eq. 5.15 with  $R_d = 12,000(1.1) = 13,200 \Omega$  to get

$$A_{cm} = \frac{(1500)(13,200) - (12,000)(1500)}{1500(1500 + 13,200)} \\ = 0.08163.$$

Then use the difference mode gain equation in Eq. 5.15 with  $R_d = 12,000(1.1) = 13,200 \Omega$  to get

$$A_{dm} = \frac{13,200(1500 + 12,000) + 12,000(1500 + 13,200)}{2(1500)(1500 + 13,200)} \\ = 8.0408.$$

The CMRR (Eq. 5.20) is thus


$$\text{CMRR} = \left| \frac{8.0408}{0.08163} \right| = 98.5.$$



Example 5.7 analyzes a noninverting-amplifier circuit that employs the more realistic op amp model.

### EXAMPLE 5.7 Analyzing a Noninverting-Amplifier Circuit using a Realistic Op Amp Model

Here we analyze the noninverting amplifier designed in Example 5.5 using the realistic op amp model in Fig. 5.18. Assume that the open-loop gain  $A = 50,000$ , the input resistance  $R_i = 100 \text{ k}\Omega$ , and the output resistance  $R_o = 7.5 \text{ k}\Omega$ . The circuit is shown in Fig. 5.21; note that there is no load resistance at the output.

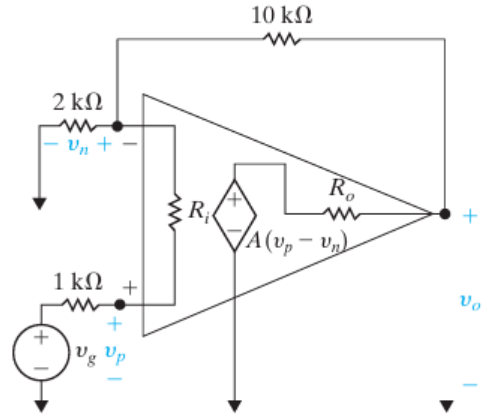

**Figure 5.21** ▲ The difference amplifier from Example 5.5, using a realistic op amp model with  $A = 50,000$ ,  $R_i = 100 \text{ k}\Omega$ , and  $R_o = 7.5 \text{ k}\Omega$ .

## 98 The Operational Amplifier

- Calculate the ratio of the output voltage to the source voltage,  $v_o/v_g$ .
- Find the voltages at the op amp input terminals  $v_n$  and  $v_p$ , with respect to the common node, when  $v_g = 1 \text{ V}$ .
- Find the voltage difference at the op amp input terminals,  $(v_p - v_n)$ , when  $v_g = 1 \text{ V}$ .
- Find the current in the signal source,  $i_g$ , when the voltage of the source  $v_g = 1 \text{ V}$ .

### Solution

) Using Eq. 5.27,

$$\frac{v_o}{v_g} = \frac{10 \text{ k} + 2 \text{ k} + \frac{(2 \text{ k})(7.5 \text{ k})}{(100 \text{ k})(50,000)}}{2 \text{ k} + \frac{7.5 \text{ k}}{50,000} \left( 1 + \frac{2 \text{ k} + 1 \text{ k}}{100 \text{ k}} \right) + \frac{1}{50,000(100 \text{ k})} [(10 \text{ k})(2 \text{ k}) + (10 \text{ k} + 2 \text{ k})(100 \text{ k} + 1 \text{ k})]} = 5.9988.$$

Note how close this value is to the gain of 6 specified and achieved in Example 5.5 using the ideal op amp model.

- b) From part (a), when  $v_g = 1 \text{ V}$ ,  $v_o = 5.9988 \text{ V}$ . Now use Eq. 5.23 to solve for  $v_n$  in terms of  $v_o$  and  $v_g$ :

$$\begin{aligned} v_n \left( \frac{1}{2 \text{ k}} + \frac{1}{1 \text{ k} + 100 \text{ k}} + \frac{1}{10 \text{ k}} \right) &= \frac{1}{100 \text{ k} + 1 \text{ k}} + \frac{5.9988}{10 \text{ k}}; \\ v_n &= 0.999803 \text{ V}. \end{aligned}$$

Use Eq. 5.25 to solve for  $v_p$ :

$$\begin{aligned} v_p &= \frac{R_g(v_n - v_g)}{R_i + R_g} + v_g = \frac{1 \text{ k}(0.999803 - 1)}{100 \text{ k} + 1 \text{ k}} + 1 \\ &= 0.999996 \text{ V}. \end{aligned}$$

- c) Using the results from part (b), we find that the voltage difference at the op amp input terminals is

$$v_p - v_n = 192.895 \mu\text{V}.$$

While this voltage difference is very small, it is not zero, as we assume when using the ideal op amp model.

- d) The current in the signal source is the current in the resistor  $R_g$ . Using Ohm's law,

$$i_g = \frac{v_g - v_p}{R_g} = \frac{1 - 0.999996}{1000} = 3.86 \text{ nA}.$$

This is also the current into the noninverting op amp terminal. It is very small but is not zero, as we assume when using the ideal op amp model.